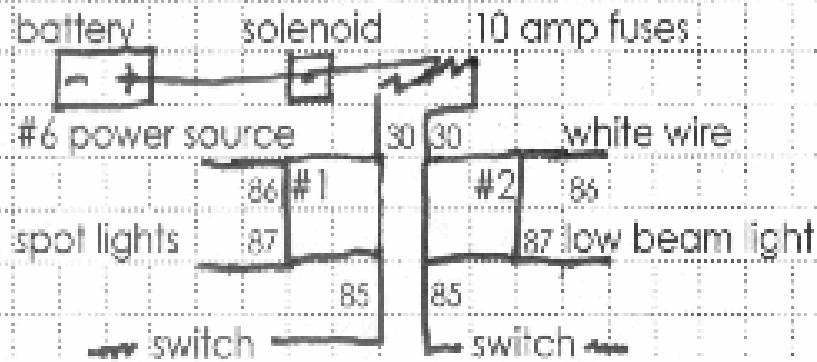



#1 Best system --- Full control of the individual lights. A failure in one will not affect the other. #2 Second best --- Same as #1 except for a single on/off switch for both sets of lights. #3 Good set up --- Same as #1 & #2 except for a single fuse, relay, and switch for both sets of lights. A failure will shut down both sets of lights. #4 Simple set up --- Powered thru a fuse, switch, and to the spot lights. On/off with the ignition key. The switch must be compatible with the ampage used. #5 Simplest set up --- Power from the #6 power source wire to the lights. On/off with the ignition key. Note: High beam, parking, and tail lights all operate as normal with all 5 systems. Locate the fuses near the battery and the relays in the headlight housing. The # 6 power source wire ( orange/blue tracer) is in a connector with a ground wire (black/white) in the headlight housing. Suggested locations for the switches are just under the triple tree and on the right handle bar switch housing. On #1, 2, & 3 diagrams the relays are live at the battery side and powered when the key is on by either #6 or white wires. The switches complete the ground for the relays to allow voltage to the lights. Relay - 12V/30A. #30 Battery supply, #85 for either ground or switch to ground, #86 key on to either #6 power source or white wire, #87 to either spots or low beam

# Wiring systems for low beam light and spot lights


#1 Dual relays and switches




#2 Dual relays & single switch

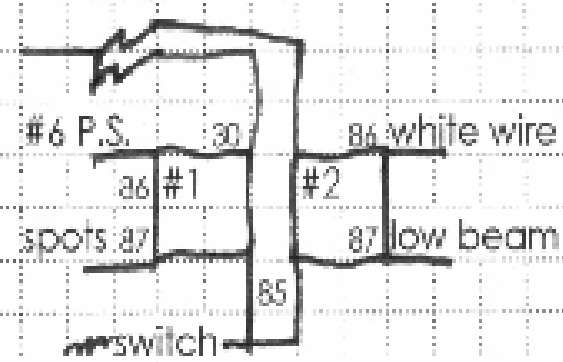

#3 Single relay and switch

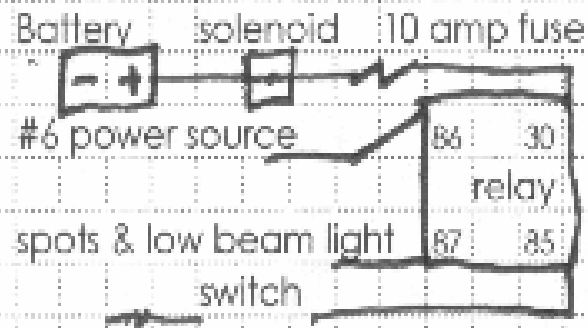

#4 Fused with switch

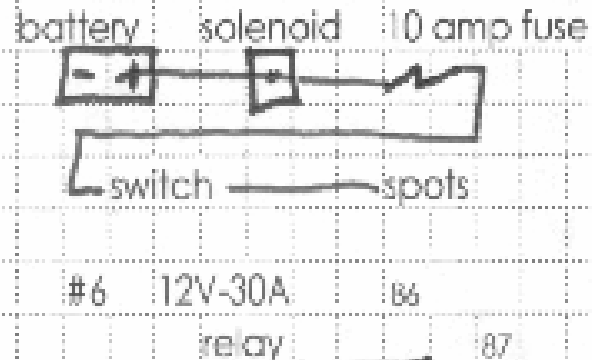

#5 Simplest set up

